

# EE5303 Microwave Electronics

## Part 2


### Tutorial Q&As

*Edited by En-Xiao Liu, 12 Oct 2022*

This set of tutorial material should be used for the sole purpose of supplementing the study of Part 2 of EE5303.  
Questions are mainly taken or adapted from the 3 designated reference textbooks.

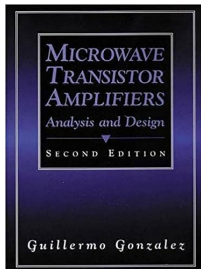**All copyrights belong to the original authors/publishers.**

- *Please study and grasp the key points covered in the four Lecture notes.*
  - *Please try all the examples in the lecture notes at least once.*
- *Do not hesitate to talk to your classmates, Prof. Guo, me, or our GAs, if you need help.*



# Q1

[Gonzalez, p.16] (adapted)

The propagation constants of the transmission lines in Fig. 1.3.6 is  $\beta$ .

Use the Transmission Line Equation to find out the expression (in terms of  $\beta, d, l, Z_0$  and/or  $Z_L$ ) for the input impedance  $\mathbf{Z}$  and reflection coefficient  $\Gamma$  for four cases: (a), (b), (c) and (d).

## Key Formulae





### Lossless

When  $Z$  is normalized to the characteristic impedance  $Z_0$

$$Z_{in}(\ell) = Z_0 \frac{Z_L + j Z_0 \tan(\beta \ell)}{Z_0 + j Z_L \tan(\beta \ell)} \quad \Gamma_0 = \frac{z - 1}{z + 1}$$


$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} \quad \Gamma_{IN}(d) = \Gamma_0 e^{-j2\beta d}$$

$$z_{IN}(d) = \frac{1 + \Gamma_{IN}(d)}{1 - \Gamma_{IN}(d)}$$

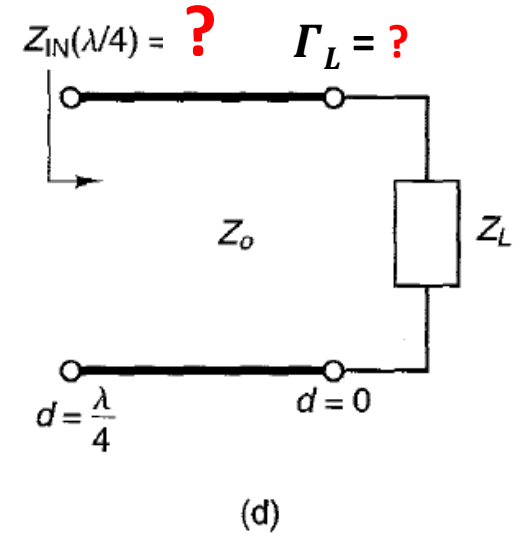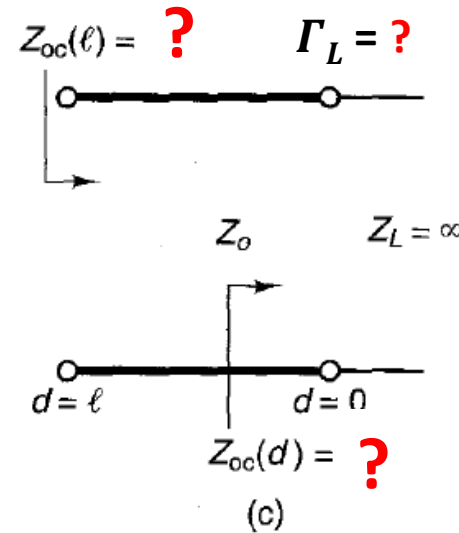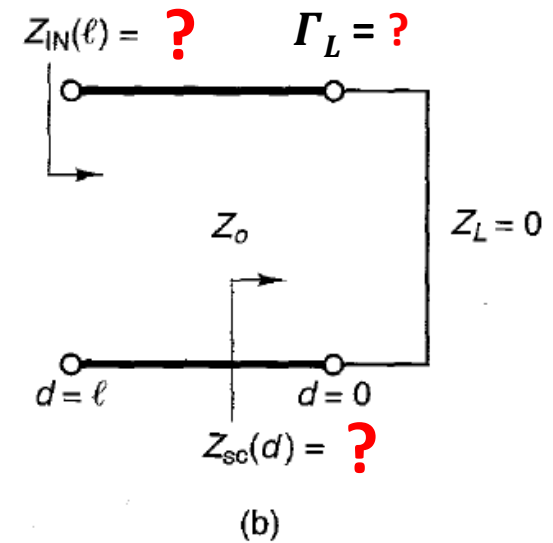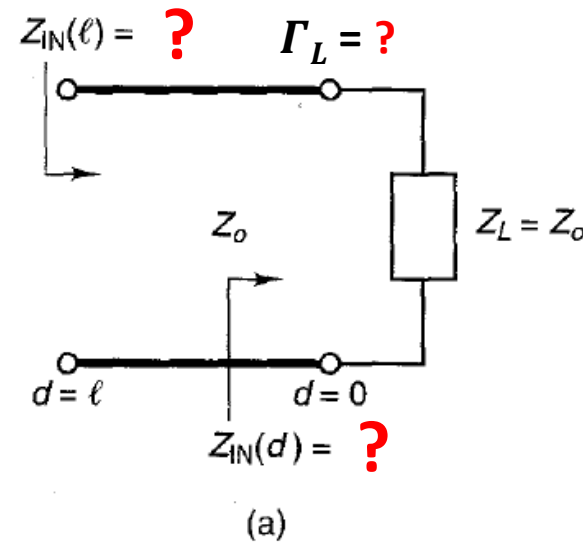

**Figure 1.3.6** (a) The matched transmission line; (b) the short-circuited transmission line; (c) the open-circuited transmission line; (d) the quarter-wave transmission line.

# Q1-Ans

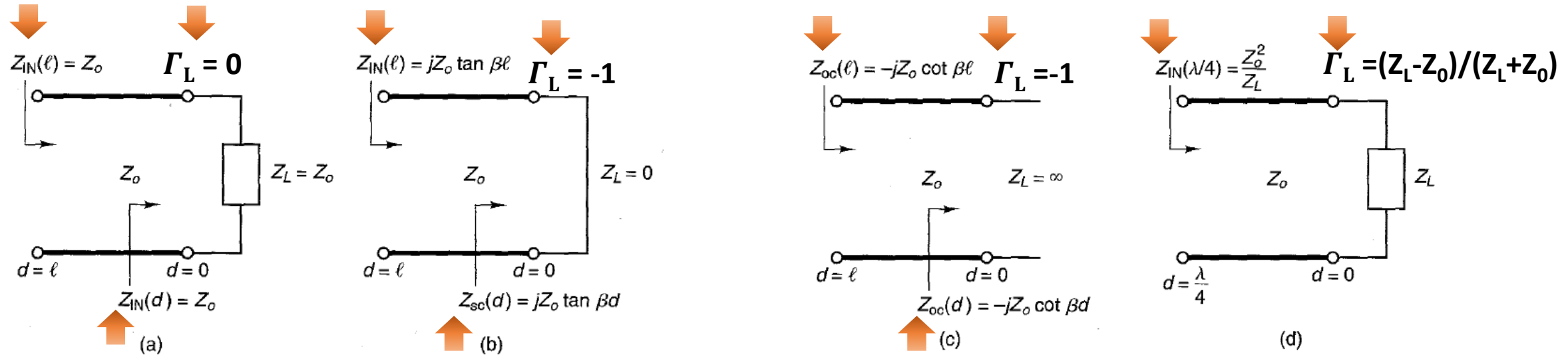

**Figure 1.3.6** (a) The matched transmission line; (b) the short-circuited transmission line; (c) the open-circuited transmission line; (d) the quarter-wave transmission line.

# Q2

\*\*\* Q2 & the info. below are for reference only, which is **NOT** in the EE5303 syllabus.

## Bipolar Transistors & Conversions of y parameters


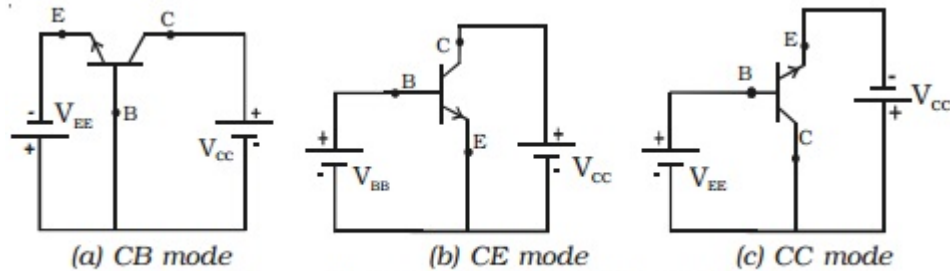
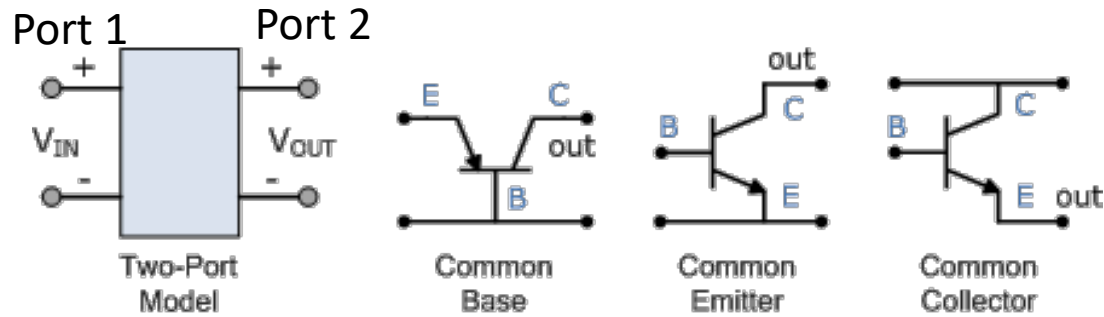


Fig Three modes of transistor circuit

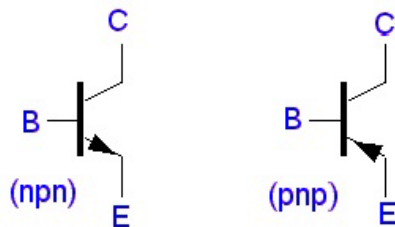

CB, BE, CC  
Conversion between Common-Base, Common-Emitter, and Common-Collector y Parameters

$$\begin{aligned}
 y_{11,e} &= y_{11,b} + y_{12,b} + y_{21,b} + y_{22,b} = y_{11,c} \\
 y_{12,e} &= -(y_{12,b} + y_{22,b}) = -(y_{11,c} + y_{12,c}) \\
 y_{21,e} &= -(y_{21,b} + y_{22,b}) = -(y_{11,c} + y_{21,c}) \\
 y_{22,e} &= y_{22,b} = y_{11,c} + y_{12,c} + y_{21,c} + y_{22,c} \\
 y_{11,b} &= y_{11,e} + y_{12,e} + y_{21,e} + y_{22,e} = y_{22,c} \\
 y_{12,b} &= -(y_{12,e} + y_{22,e}) = -(y_{21,c} + y_{22,c}) \\
 y_{21,b} &= -(y_{21,e} + y_{22,e}) = -(y_{12,c} + y_{22,c}) \\
 y_{22,b} &= y_{22,e} = y_{11,c} + y_{12,c} + y_{21,c} + y_{22,c} \\
 y_{11,c} &= y_{11,e} = y_{11,b} + y_{12,b} + y_{21,b} + y_{22,b} \\
 y_{12,c} &= -(y_{11,e} + y_{12,e}) = -(y_{11,b} + y_{21,b}) \\
 y_{21,c} &= -(y_{11,e} + y_{21,e}) = -(y_{11,b} + y_{12,b}) \\
 y_{22,c} &= y_{11,e} + y_{12,e} + y_{21,e} + y_{22,e} = y_{11,b}
 \end{aligned}$$

[Gonzalez, p.63]

# Q2

[Gonzalez, p.91]

1.27 The common-emitter  $S$  parameters of a GaAs FET at  $f = 10$  GHz are

$$S_{11} = 0.73 \angle -128^\circ$$

$$S_{21} = 1.73 \angle 73^\circ$$

$$S_{12} = 0.045 \angle 114^\circ$$

$$S_{22} = 0.75 \angle -52^\circ$$

Determine the common-base and common-collector  $S$  parameters.

# Q2-Ans

1.27) CONVERT THE CE  $S$  PARAMETERS TO CE  $y$  PARAMETERS (SEE FIG. 1.8.1)

THAT IS:  $y_{11,e} = 0.016 + j0.034$   $y_{12,e} = 0.00141 - j0.0272(10^{-3})$

$y_{21,e} = 0.04 - j0.036$   $y_{22,e} = 0.00363 + j0.0079$

USE THE RELATIONS IN FIG. 1.8.1b TO CALCULATE THE CB AND CC  $y$  PARAMETERS. THAT IS,

$y_{11,b} = 0.061 + j0.00587$   $y_{12,b} = -0.00503 - j0.00787$

$y_{21,b} = -0.0436 + j0.0281$   $y_{22,b} = 0.00363 + j0.0079$

AND

$y_{11,c} = 0.016 + j0.034$   $y_{12,c} = -0.0174 - j0.034$

$y_{21,c} = -0.056 + j0.002$   $y_{22,c} = 0.061 + j0.00587$

CONVERT FROM CB AND CC  $y$  PARAMETERS TO CB AND CC  $S$  PARAMETERS. THAT IS,

$$[S]_{CB} = \begin{bmatrix} 0.356 \angle -173.6^\circ & 0.243 \angle 35.41^\circ \\ 1.348 \angle -54.81^\circ & 1.198 \angle -32.7^\circ \end{bmatrix} \text{ AND } [S]_{CC} = \begin{bmatrix} 0.893 \angle -62.03^\circ & 0.764 \angle 29.68^\circ \\ 1.12 \angle -35.26^\circ & 0.176 \angle 98.35^\circ \end{bmatrix}$$



# Q3a

## Example 2.2.4

Find the input impedance, the load reflection coefficient, in a transmission line having an electrical length of  $45^\circ$ , characteristic impedance of  $50\ \Omega$ , and terminated in a load  $Z_L = 50 + j50\ \Omega$ .

[Gonzalez, p.101-105]

Q3a-Ans

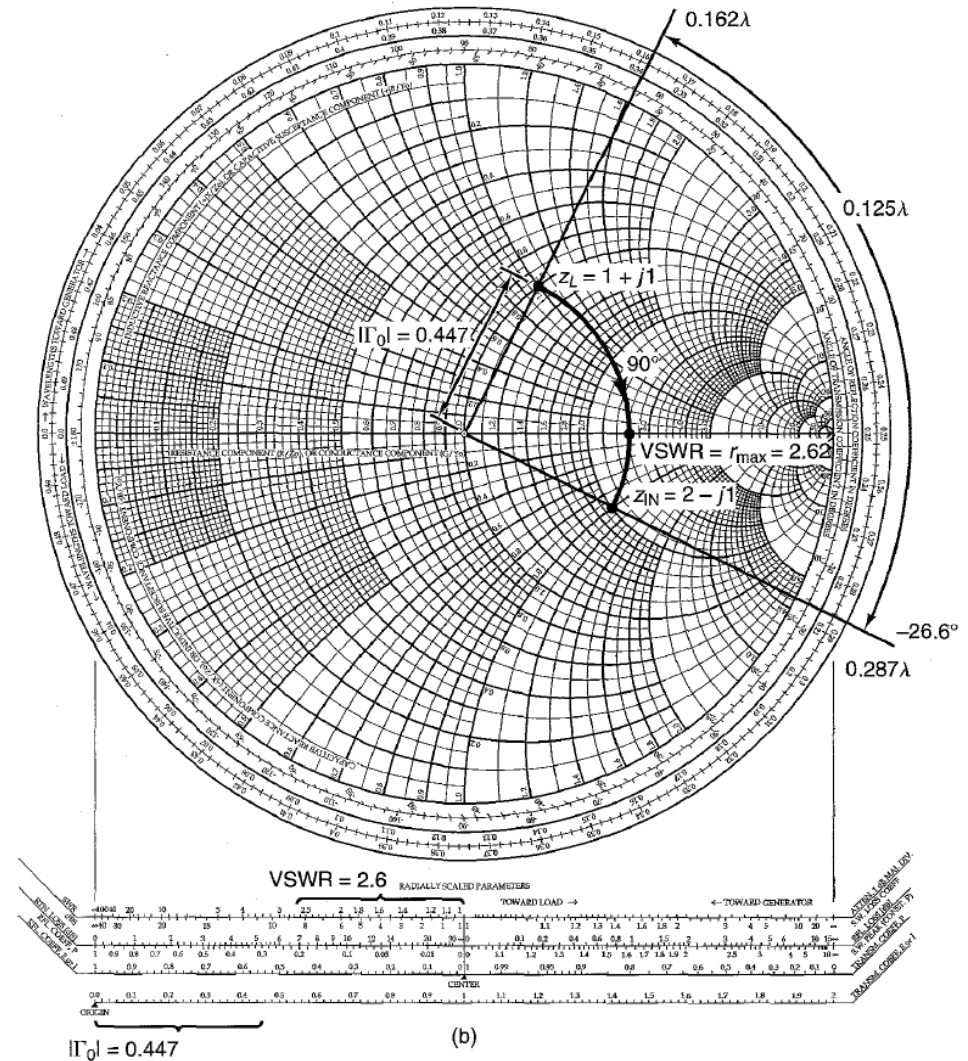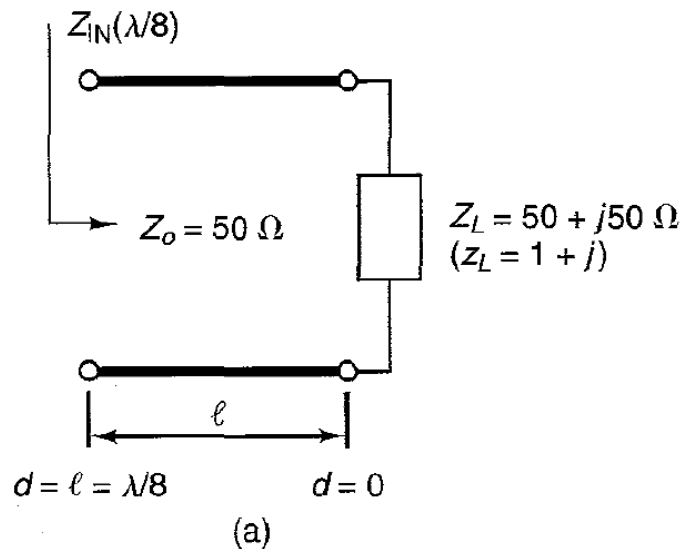

# Q3b

## Example 2.2.5

[Gonzalez, p.101-105]

(a) Determine the length  $l$  of the  $50\text{-}\Omega$  short-circuited transmission line shown in Fig. 2.2.8a so that the input impedance is  $Z_{\text{IN}}(l) = j100\text{ }\Omega$ .

(b) Determine the length  $l$  of the  $50\text{-}\Omega$  open-circuited transmission line shown in Fig. 2.2.8b so that the input impedance is  $Z_{\text{IN}}(l) = j100\text{ }\Omega$ .

## Q3b-Ans

**Solution.** (a) In the short-circuited transmission line,  $z_L = 0$ . From Fig. 2.2.8a, the length  $l$  required to transform the load impedance  $z_L = 0$  to the input impedance  $z_{\text{IN}}(l) = j100/50 = j2\text{ }\Omega$  is  $l = 0.176\lambda$ . Observe that in a short-circuited line the motion is along the edge of the chart (since  $|\Gamma| = 1$  in a short-circuited line).

The length could have been calculated using (1.3.45). That is,

$$Z_{\text{IN}}(l) = j100 = j50 \tan \beta l$$

which gives  $\tan \beta l = 2$  or  $\beta l = 63.43^\circ = 0.352\pi$ . Then

$$l = \frac{0.352\pi\lambda}{2\pi} = 0.176\lambda$$

(b) In the open-circuited transmission line,  $z_L = \infty$ . Therefore, from Fig. 2.2.8b the length  $l$  is  $0.426\lambda$  [i.e.,  $(0.5\lambda - 0.25\lambda) + 0.176\lambda = 0.426\lambda$ ].

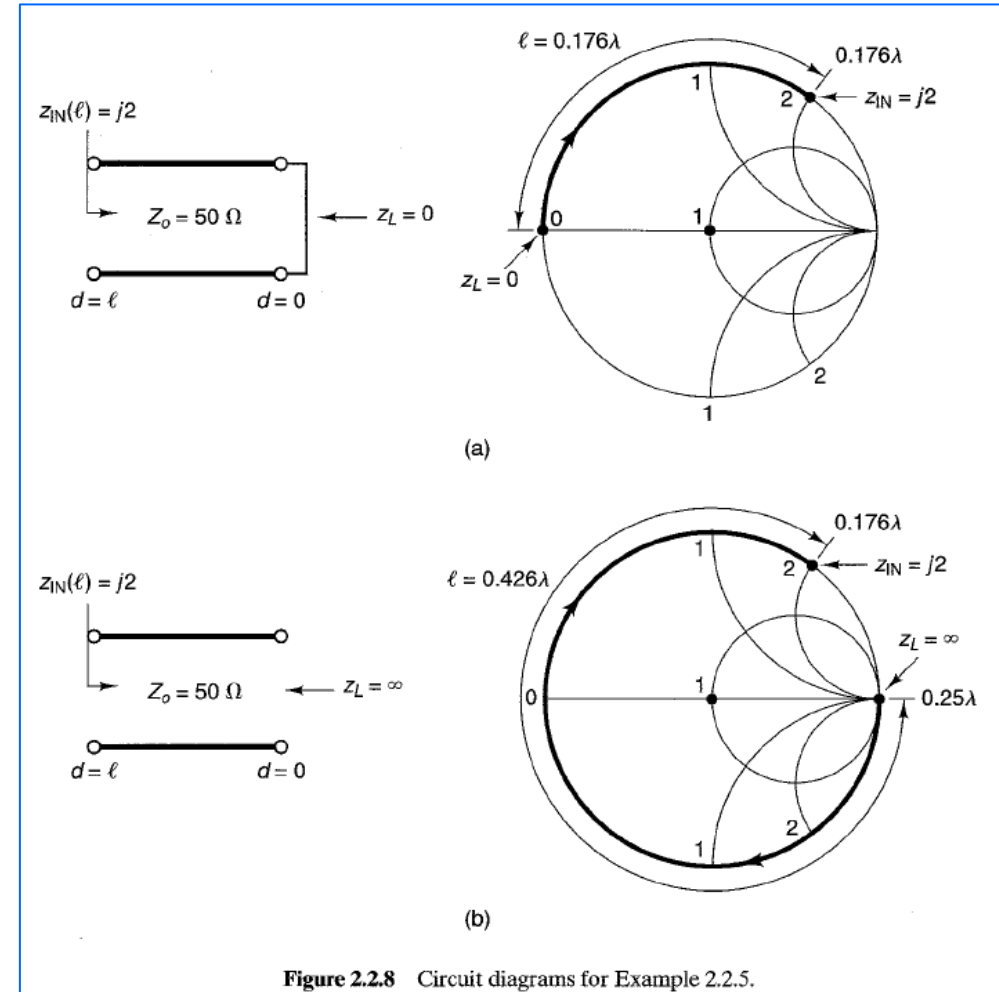


Figure 2.2.8 Circuit diagrams for Example 2.2.5.



### Example 2.2.6

[Gonzalez, p.101-105]

(a) Determine the input admittance of a short-circuited transmission line having a length of  $\lambda/8$  and  $Y_o = 1/Z_o = 20 \text{ mS}$ .

(b) Determine the input admittance of an open-circuited transmission line having a length of  $\lambda/8$  and  $Y_o = 1/Z_o = 20 \text{ mS}$ .

### Q3c-Ans

**Solution.** (a) For the short-circuited line, the load admittance is  $y_L = \infty$ . Plotting  $y_L$  in the  $Y$  Smith chart shown in Fig. 2.2.9a and rotating along the constant gamma circle  $|\Gamma| = 1$  a distance  $l = \lambda/8$ , we obtain  $y_{IN}(l) = -j$  or

$$Y_{IN}(l) = y_{IN}(l)Y_o = -j(20 \times 10^{-3}) = -j20 \text{ mS}$$

The input impedance is  $Z_{IN}(l) = 1/Y_{IN}(l) = j50 \Omega$ .

(b) In the open-circuited line, the load admittance is  $y_L = 0$ . Therefore, as shown in Fig. 2.2.9b, at  $l = \lambda/8$  we obtain  $y_{IN}(l) = j$  or

$$Y_{IN}(l) = y_{IN}(l)Y_o = j(20 \times 10^{-3}) = j20 \text{ mS}$$

The input impedance is  $Z_{IN}(l) = 1/Y_{IN}(l) = -j50 \Omega$ .

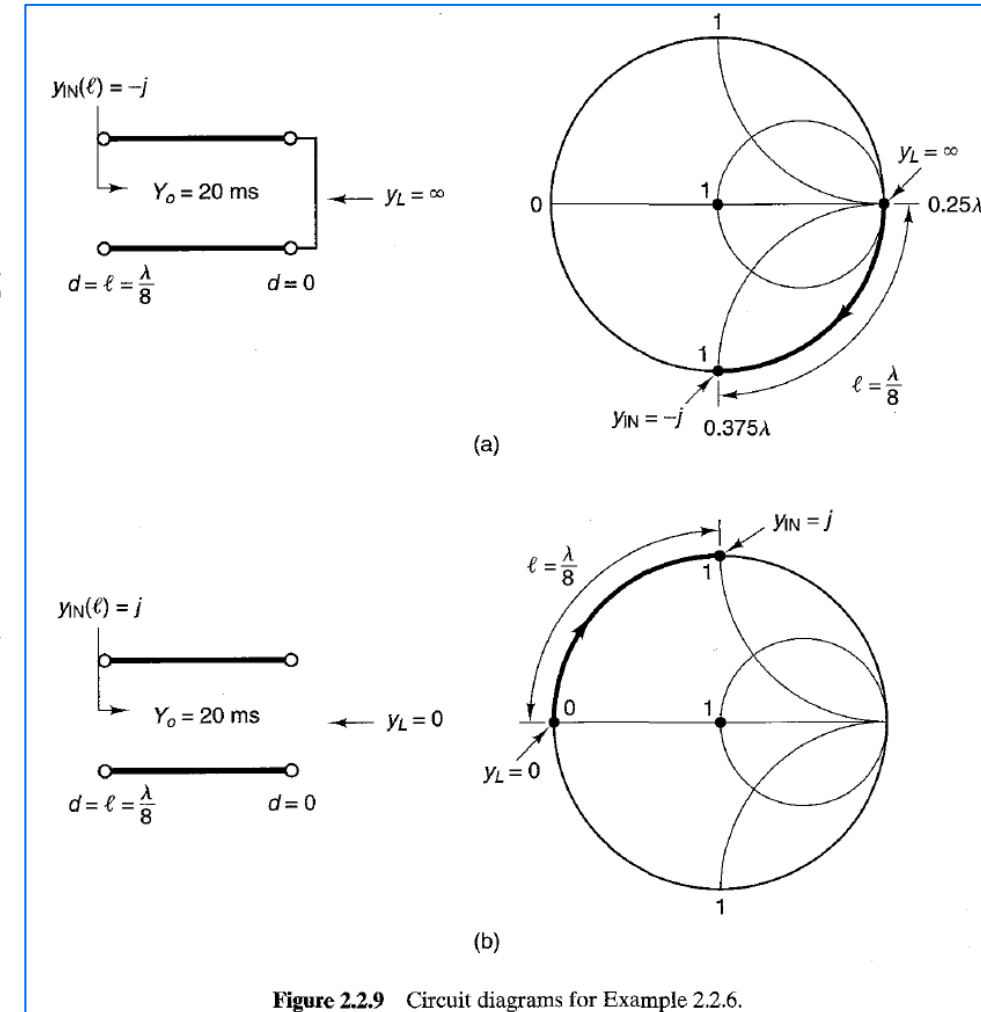


Figure 2.2.9 Circuit diagrams for Example 2.2.6.



# Q4

[Gonzalez, p.288]

**3.18** A microwave amplifier is to be designed for  $G_{TU,\max}$  using a transistor with

$$S_{11} = 0.5 \angle 140^\circ \quad S_{12} = 0$$

$$S_{21} = 5 \angle 45^\circ \quad S_{22} = 0.6 \angle -95^\circ$$

The  $S$  parameters were measured in a  $50\text{-}\Omega$  system at  $f = 900\text{ MHz}$ ,  $V_{CE} = 15\text{ V}$ , and  $I_C = 15\text{ mA}$ .

- (a) Determine  $G_{TU,\max}$ .
- (b) Design two different microstrip matching networks.
- (c) Draw the constant gain circle for  $G_L = 1\text{ dB}$ .
- (d) If the  $S$  parameters at  $1\text{ GHz}$  are

$$S_{11} = 0.48 \angle 137^\circ \quad S_{12} = 0$$

$$S_{21} = 4.6 \angle 48^\circ \quad S_{22} = 0.57 \angle -99^\circ$$


calculate the gain  $G_T$  at  $1\text{ GHz}$  for the designs in part (b).

# Q4-Ans

3.18)(a)  $G_{L, \max} = \frac{1}{1 - (0.5)^2} = 1.33$  OR 1.25 dB,  $G_{L, \max} = \frac{1}{1 - (0.6)^2} = 1.563$  OR 1.94 dB

$G_o = |S_{21}|^2 = 25$  OR 13.98 dB,  $\therefore G_{TU, \max} = 1.25 + 13.98 + 1.94 = 17.2$  dB

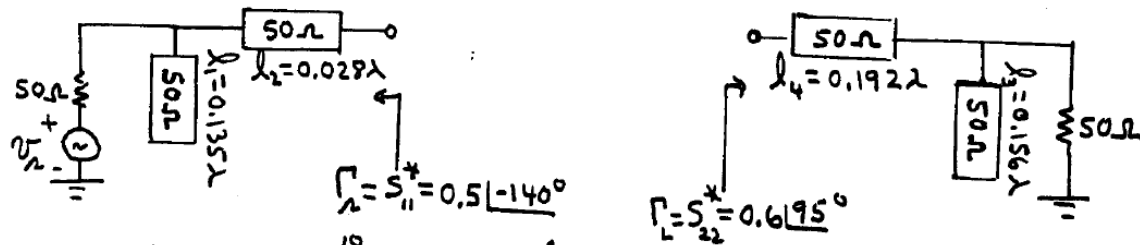(b) A MATCHING NETWORK DESIGN AT 900 MHz IS:




AT 900 MHz:  $\lambda = \frac{310}{910} = 33.3$  cm,  $l_1 = 0.135\lambda = 4.496$  cm,  $l_2 = 0.028\lambda = 0.932$  cm,  $l_3 = 0.156\lambda = 5.195$  cm,  $l_4 = 0.192\lambda = 6.394$  cm

(c)  $g_L = \frac{G_L}{G_{L, \max}} = \frac{1.259}{1.563} = 0.805$

FROM (3.4.11) AND (3.4.12):

$C_L = 0.519 \angle 95^\circ$

$\Gamma_L = 0.304$

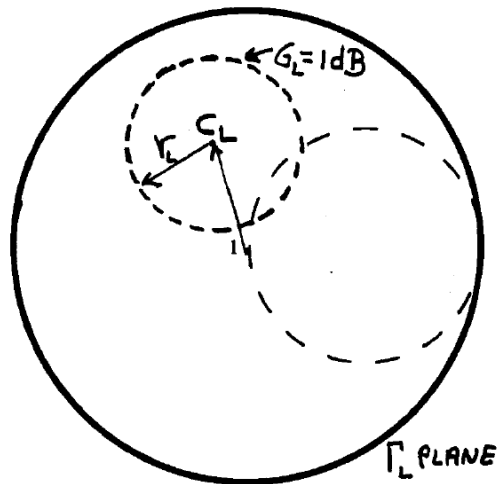


(d) LET  $\lambda' = \frac{c}{f'}$  WHERE  $f' = 1$  GHz,

AND  $\lambda = \frac{c}{f}$  WHERE  $f = 900$  MHz.

$\therefore \frac{\lambda}{\lambda'} = \frac{f'}{f}$  OR  $\lambda = \frac{f'}{f} \lambda' = \frac{10^9}{910^8} \lambda' = 1.11\lambda'$

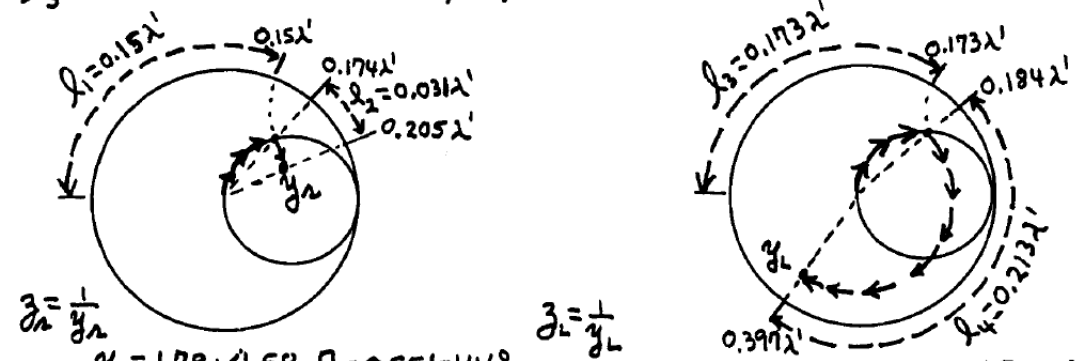$l_1 = 0.135\lambda = 0.135(1.11\lambda') = 0.15\lambda'$ ,  $l_2 = 0.028(1.11\lambda') = 0.031\lambda'$ ,  $l_3 = 0.156(1.11\lambda') = 0.173\lambda'$ ,  $l_4 = 0.192(1.11\lambda') = 0.213\lambda'$



$\therefore G_{TU} = \frac{1 - (0.55)^2}{|1 - 0.48 \angle 137^\circ (0.55 \angle -140^\circ)|^2} (4.6)^2 = \frac{1 - (0.693)^2}{|1 - 0.57 \angle -99^\circ (0.693 \angle 74.4^\circ)|^2} = 31.97$  OR 15.05 dB

# Q5

**5.15 (a)** Johnson shows that the output power of an oscillator can be approximated with the equation

[Gonzalez, p.431]

$$P_{\text{OUT}} = P_{\text{sat}}(1 - e^{-G_o P_{\text{IN}}/P_{\text{sat}}})$$

where  $P_{\text{sat}}$  is the saturated output power of the amplifier,  $P_{\text{IN}}$  is the input power, and  $G_o$  is the small-signal power gain. Show that the maximum oscillator power [ $P_{\text{osc}}(\text{max})$ ] is given by

$$P_{\text{osc}}(\text{max}) = P_{\text{sat}} \left( 1 - \frac{1}{G_o} - \frac{\ln G_o}{G_o} \right)$$

*Hint:* The maximum oscillator power occurs at the point of maximum  $P_{\text{OUT}} - P_{\text{IN}}$ , or where

$$\frac{\partial P_{\text{OUT}}}{\partial P_{\text{IN}}} = 1$$

- (b) A GaAs FET has  $G_o = 7.5$  dB with  $P_{\text{sat}} = 1$  W. Calculate the maximum oscillator power.
- (c) Draw a typical  $P_{\text{osc}}/P_{\text{sat}}$  versus  $G_o$  plot.

# Q5-Ans

$$5.15) (a) P_{out} = P_{sat} (1 - e^{-G_0 P_{in}/P_{sat}}) \quad (1)$$

MAXIMUM OSCILLATOR POWER OCCURS WHEN  $P_{out} - P_{in}$  IS A MAXIMUM, OR  $\frac{\partial P_{out}}{\partial P_{in}} = 1$ . SINCE

$$\frac{\partial P_{out}}{\partial P_{in}} = P_{sat} \left( -\frac{G_0}{P_{sat}} \right) \left( e^{-G_0 P_{in}/P_{sat}} \right) = G_0 e^{-G_0 P_{in}/P_{sat}} = 1$$

$$\text{THEN, } e^{-G_0 P_{in}/P_{sat}} = \frac{1}{G_0} \quad \text{OR} \quad P_{in} = P_{sat} \frac{\ln G_0}{G_0} \quad (2)$$

SUBSTITUTING (2) INTO (1),  $P_{out}$  CAN BE EXPRESSED AS:

$$P_{out} = P_{sat} \left( 1 - \frac{1}{G_0} \right) \quad (3)$$


FROM (3) AND (2), THE MAXIMUM OSCILLATOR POWER ( $P_{osc(max)}$ ) IS

$$P_{osc(max)} = P_{out} - P_{in} = P_{sat} \left( 1 - \frac{1}{G_0} - \frac{\ln G_0}{G_0} \right)$$

$$(b) G_0 = 7.5 \text{ dB} \quad \text{OR} \quad 5.623$$

$$P_{sat} = 1 \text{ W}$$
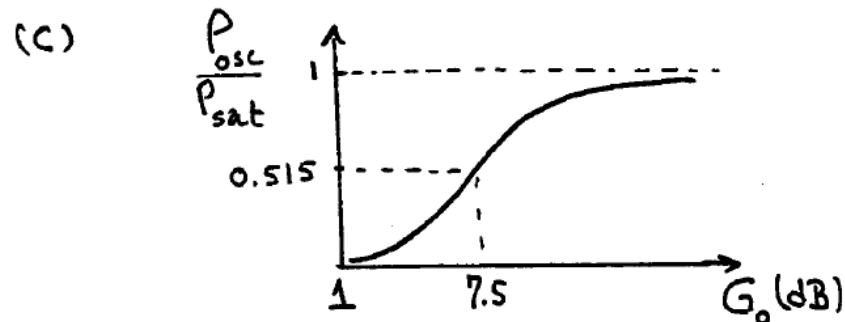
$$P_{osc(max)} = 1 \left( 1 - \frac{1}{5.623} - \frac{\ln 5.623}{5.623} \right) = 0.515 \text{ W}$$



# Q6

- 5.4 A negative-resistance device can be modeled by the parallel combination of a capacitor and a negative conductance, as shown in Fig. P5.4. The amplitude dependence of the negative conductance is given by (5.2.30).

[Gonzalez, p.428]

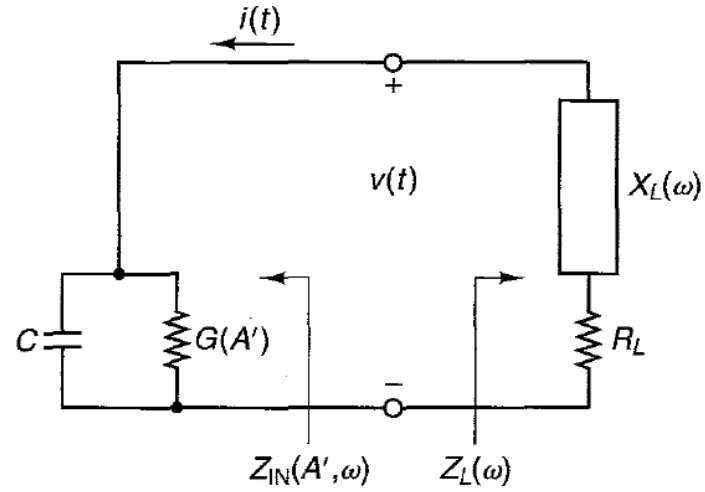


Figure P5.4

- (a) Show that a stable oscillation at  $\omega = \omega_o$  occurs when

$$R_L = \frac{-G(A')}{G^2(A') + \omega^2 C^2}$$

$$X_L(\omega_o) = \frac{\omega C}{G^2(A') + \omega^2 C^2}$$

- (b) Show that the oscillator power is a maximum when

$$G_L = \frac{G_0}{3}$$

where  $Y_L(\omega) = G_L + jB_L(\omega)$ .

## Q6-Ans

$$5.4)_{(a)} Z_{IN}(A', \omega) = \frac{1}{G(A') + j\omega C} = \frac{G(A')}{G^2(A') + \omega^2 C^2} + j \frac{-\omega C}{G^2(A') + \omega^2 C^2}$$

$$\therefore R_{IN}(A', \omega) = \frac{G(A')}{G^2(A') + \omega^2 C^2} \text{ AND } X_{IN}(A', \omega) = \frac{-\omega C}{G^2(A') + \omega^2 C^2}$$

Based on the oscillation conditions, A STABLE OSCILLATION OCCURS

$$R_L = -R_{IN}(A', \omega) = \frac{-G(A')}{G^2(A') + \omega^2 C^2}$$

$$X_L = -X_{IN}(A', \omega) = \frac{\omega C}{G^2(A') + \omega^2 C^2}$$

$$(b) P = \frac{1}{2} |V|^2 |G(A')| = \frac{1}{2} A'^2 G_0 (1 - A'/A'_m), \frac{\partial P}{\partial A'} = \frac{G_0}{2} (2A' - \frac{3A'^2}{A'_m}) = 0$$

OR  $A' \equiv A_{0, \max} = \frac{2}{3} A'_m$ . AT  $A' = A_{0, \max}$  THE VALUE OF  $G_{IN}(A')$  IS:

$$G_{IN}(A_{0, \max}) = -G_0/3. \text{ THEREFORE: } G_L = G_0/3.$$

# Q7

4.13 Consider the LNB shown in Fig. P4.13. Calculate the total noise figure and the available gain.

[Gonzalez, p.377]

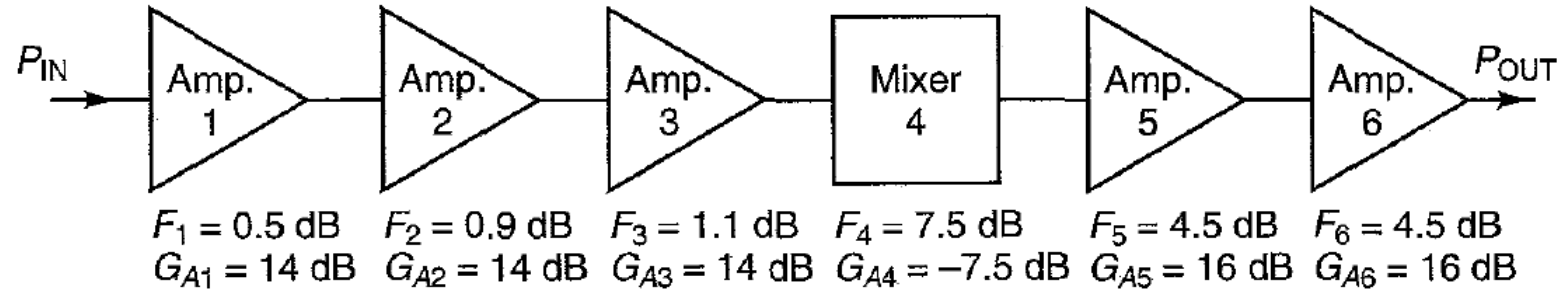


Figure P4.13

## Q7-Ans

$$4.13) G_A(\text{dB}) = 14 + 14 + 14 - 7.5 + 16 + 16 = 66.5 \text{ dB}$$

THE NOISE FIGURE OF THE LNB IS DETERMINED BY THE NOISE FIGURE OF THE LNA (I.E., THE FIRST 3 AMPLIFIERS).


$$F = F_1 + \frac{F_2 - 1}{G_{A1}} + \frac{F_3 - 1}{G_{A1}G_{A2}} = 10^{0.05} + \frac{10^{0.09} - 1}{10^{1.4}} + \frac{10^{0.11} - 1}{10^{1.4}10^{1.4}} = 1.131 \text{ or } 0.54 \text{ dB}$$

THE CONTRIBUTION TO  $F$  FROM THE MIXER, AMP. 5, AND AMP. 6 IS NEGLECTIBLE.





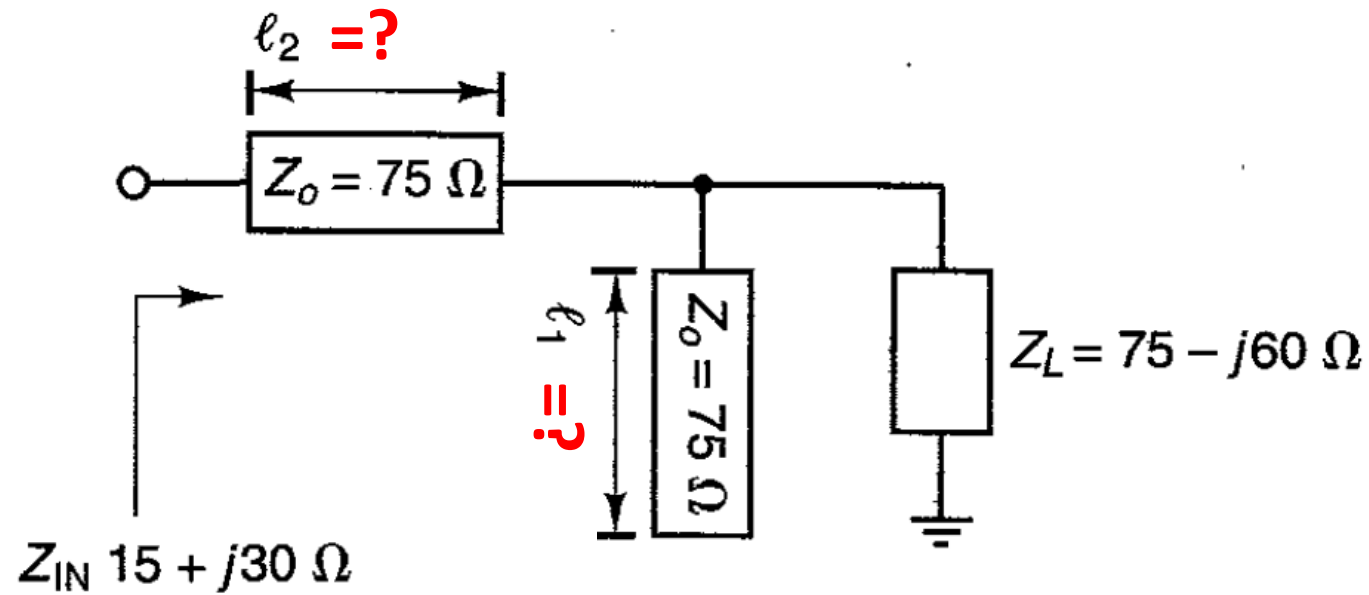Q8

Design a microstrip matching network to transform the load  $Z_L = 75 - j60 \Omega$  to an input impedance of value  $Z_{IN} = 15 + j30 \Omega$ . The characteristic impedance is  $Z_o = 75 \Omega$



# Q8-Ans

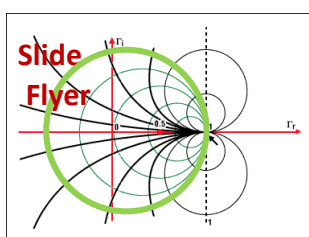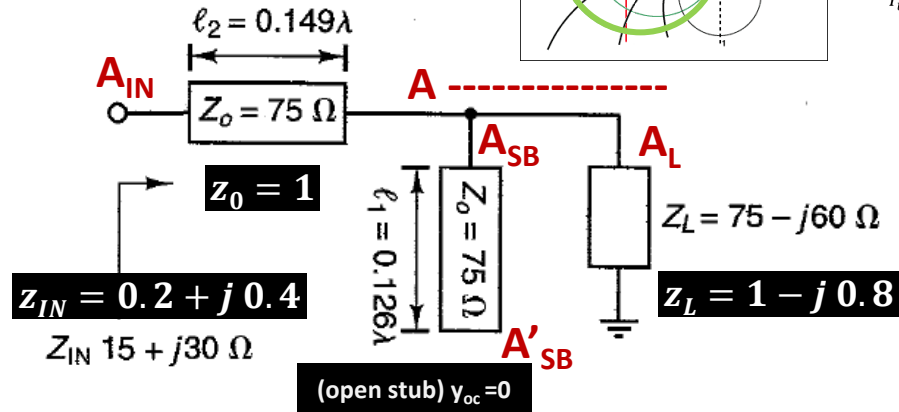


**Lossless**  
Transmission line impedance equation

$$Z_{in}(d) = Z_0 \frac{Z_L + jZ_0 \tan(\beta d)}{Z_0 + jZ_L \tan(\beta d)}$$

$$Y_{in}(d) = Y_0 \frac{Y_L + jY_0 \tan(\beta d)}{Y_0 + jY_L \tan(\beta d)}$$

$$\Gamma(d) = \Gamma_L e^{-j2\beta d} = |\Gamma_L| e^{j(\theta_L - 2\beta d)}$$

$$\beta = \frac{2\pi}{\lambda}$$

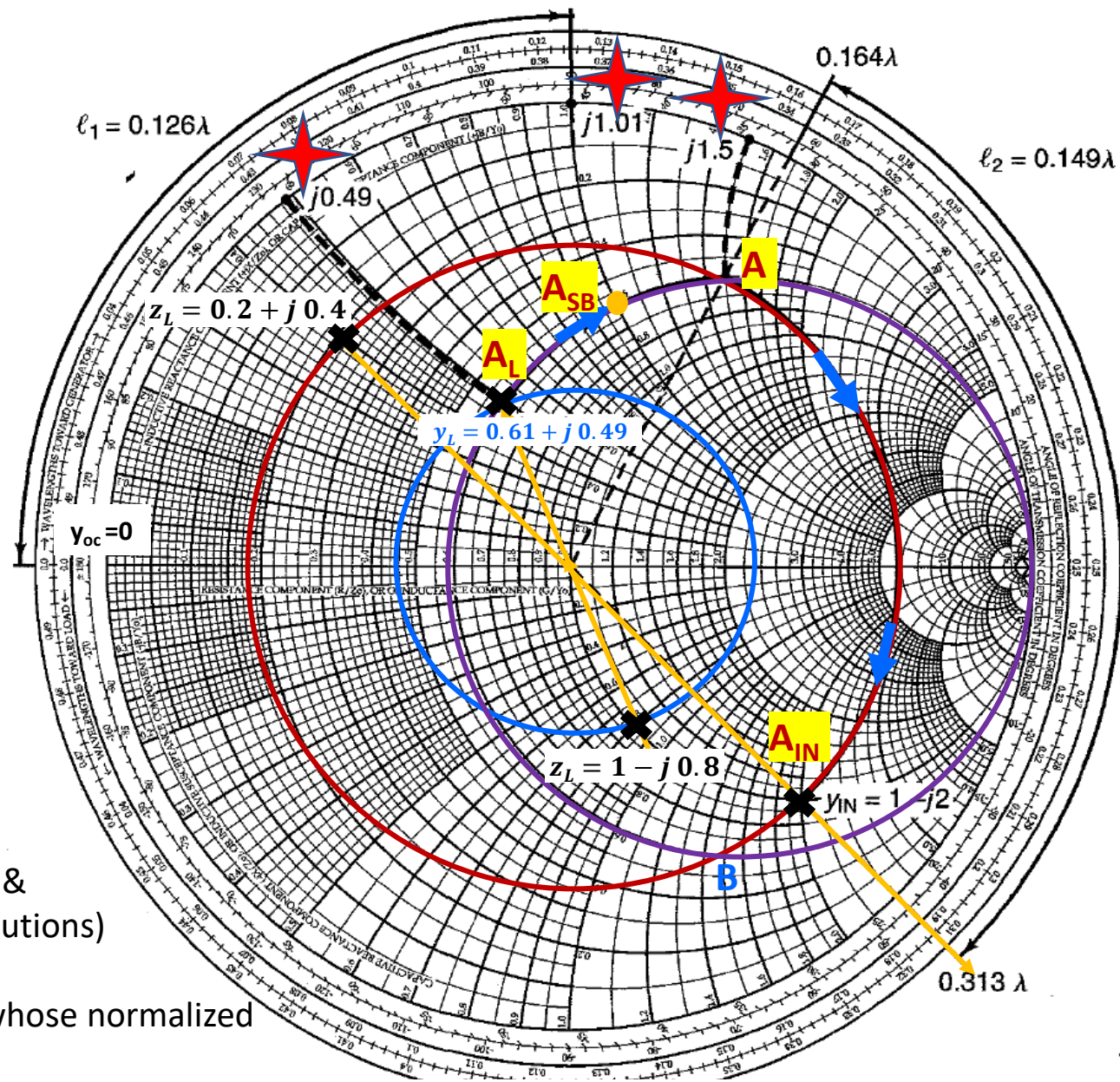

**S0:** normalization (by  $Z_0$ )

**S1:** {ride on the  $|\Gamma|$  flyers}

- (i) draw the constant  $|\Gamma|$  circle, passing through  $z_L$  (!!!bye-bye)  
read  $y_L$  at the other end of the diameter (the flyer & the slide)

$$y_L = 0.61 + j0.49 \text{ (at } A_L)$$

$$y_{IN} = 1.0 - j2.0 \text{ (at } A_{IN})$$

- (ii) repeat (i) for  $z_{IN}$  and we get

**S2:** {build the bridge to travel from  $A'$  to  $A''$ }

- (i) draw the constant conductance  $g = \text{Re}(y_L) = 0.61$  circle crossing  $A_L$  & intersecting with  $|\Gamma(y_{IN})|$  circle at two points A & B (two basic solutions)

Read  $A \rightarrow y_A = 0.61 + j1.5$  (see the flyer & the slide)

- (ii) from  $A_L [\rightarrow y_L = 0.61 + j0.49]$  to A via  $A_{SB} \rightarrow$  the shunt stub  $l_2$ , whose normalized admittance  $y_{SB} = j(1.50 - 0.49) = j1.01$

**S3:** Read, towards the generator, the length of the Transmission lines

$l_1$  (from A clockwise to  $A_{IN}$ ) and  $l_2$  (from  $A'_{SB}$  ( $y_{oc} = 0$ ) to  $A_{SB} \rightarrow$  it's a slide)

**Example 4.7.3**

Design a 1-W (or 30-dBm) GaAs FET power amplifier for linear operation at 4 GHz. The input signal power is  $-5$  dBm.

**Solution.** The required power gain of the power amplifier is

$$G_p(\text{dB}) = P_{\text{OUT}}(\text{dBm}) - P_{\text{IN}}(\text{dBm}) = 30 - (-5) = 35 \text{ dB}$$

For this design we selected the transistors from the *Hewlett-Packard Communications Components—GaAs & Silicon Products Designer's Catalog*. The transistors selected, with some pertinent data at 4 GHz, are listed in Fig. 4.7.16a. Figure 4.7.16a shows that the ATF44101 transistor can provide linear amplification with  $G_p = 10$  dB and an output power of 1 W (or 30 dBm) at 4 GHz.

The required power gain of 35 dB can be obtained using three-stages, as shown in Fig. 4.7.16b. The gain and power levels of each stage are indicated in Fig. 4.7.16b.

The power gain of the three-stage amplifier in Fig. 4.7.16b is


$$G_p = G_{p1} + G_{p2} + G_{p3} = 14 + 11 + 10 = 35 \text{ dB}$$

Therefore, the output power is

$$P_{\text{out}}(\text{dBm}) = P_{\text{in}}(\text{dBm}) + G_p = -5 + 35 = 30 \text{ dBm (or 1 W)}$$

Q9-Ans

Transistor	$Q$ point	$G_p$	$P_1$ dB	$G_1$ dB
ATF44101	9 V, 500 mA	10	32 dBm	9
ATF45101	9 V, 250 mA	11	29 dBm	10
ATF25570	5 V, 5 mA	14	20.5 dBm	13

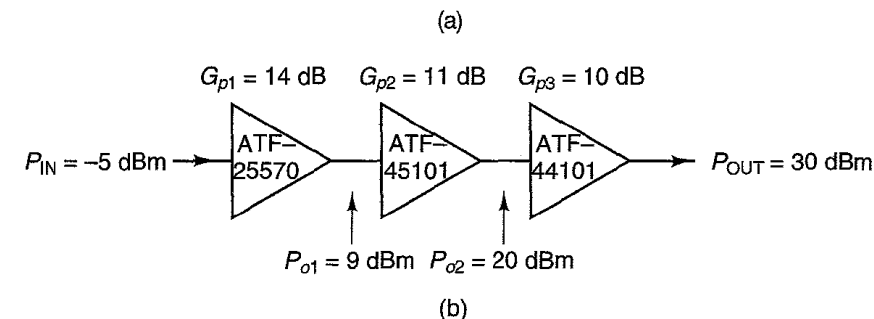

**Figure 4.7.16** (a) Transistors selected and some pertinent data at 4 GHz; (b) a 1-W, three-stage, linear power amplifier at 4 GHz.

**3.17** The scattering parameters of a GaAs FET in a 50- $\Omega$  system are

$$S_{11} = 2.3 \angle -135^\circ$$

$$S_{12} = 0$$

$$S_{21} = 4 \angle 60^\circ$$

$$S_{22} = 0.8 \angle -60^\circ$$

- (a) Determine the unstable region in the Smith chart and construct the constant-gain circle for  $G_s = 4$  dB.
- (b) Design the input matching network for  $G_s = 4$  dB with the greatest degree of stability.
- (c) Draw the complete ac amplifier schematic.



# Q10-Ans

3.17) (a) THE INPUT RESISTANCE IS CALCULATED AS FOLLOWS :

$$\Gamma_{IN} = S_{11} = 2.3 \angle -135^\circ, \quad Z_{IN} = 50(-0.45 - j0.34) = -22.48 - j17.04 \Omega$$

$Z_{IN}$  CAN ALSO BE CALCULATED USING THE SMITH CHART.

$$\text{PLOT } \frac{1}{S_{11}^*} = 0.435 \angle 135^\circ \text{ AND READ } Z_{IN} = 50(-0.45 - j0.34) = -22.5 - j17 \Omega$$


$$\text{FOR } G_n = 4 \text{ dB}, \quad g_n = 2.512 [1 - (2.3)^2] = -10.78$$

$$\text{FROM (3.4.11) AND (3.4.12): } C_n = 0.404 \angle 135^\circ \text{ AND } \Gamma_n = 0.24$$

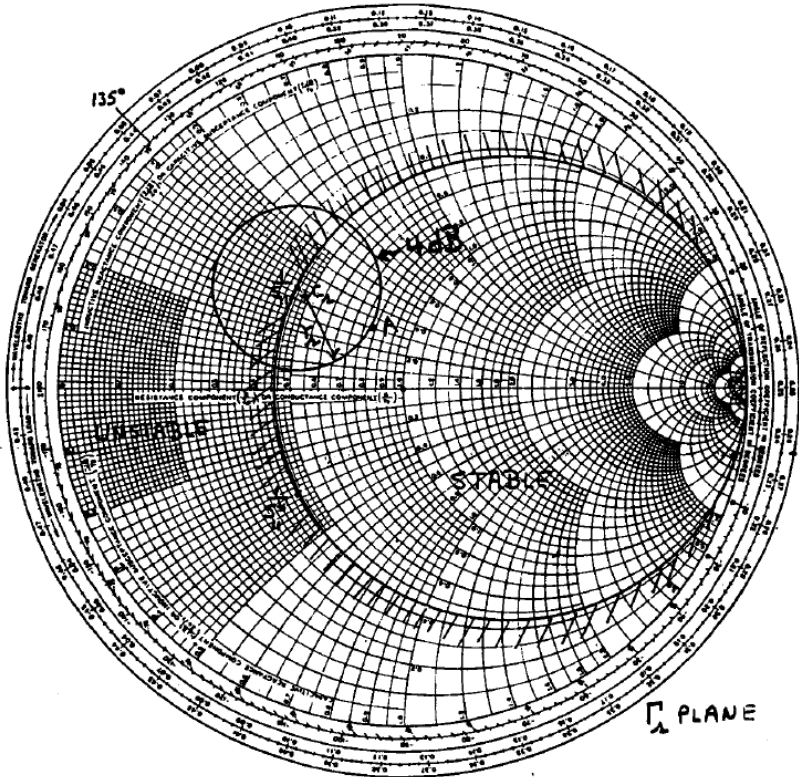
(b) AT POINT A,  $\Gamma_n$  HAS THE LARGEST REAL PART ON THE  $G_n = 4 \text{ dB}$  CIRCLE. THAT IS,

$$\Gamma_n = 0.2 \angle 115^\circ$$

THE INPUT MATCHING CIRCUIT MUST TRANSFORM  $50 \Omega$  TO  $\Gamma_n = 0.2 \angle 115^\circ$ .



(c) DESIGN FOR  $\Gamma_n = 0.2 \angle 115^\circ$  AND  $\Gamma_L = S_{22}^* = 0.8 \angle 66^\circ$ . THEN,  
 $G_n = 4 \text{ dB}$ ,  $G_o = |S_{21}|^2 = 16$  (OR  $12.04 \text{ dB}$ ),  $G_{L, \max} = \frac{1}{1 - (0.8)^2} = 2.78$  (OR  $4.4 \text{ dB}$ )  
 $\therefore G_{TW}(\text{dB}) = G_n + G_o + G_{L, \max} = 4 + 12.04 + 4.4 = 20.4 \text{ dB}$

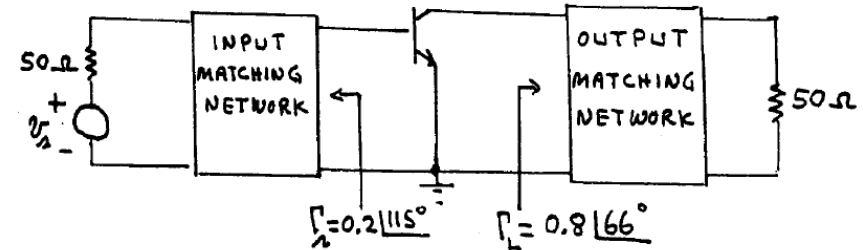



chase, that rainbow  
at the sky end



Imagination, as wings



Learning, as tools



## Summary of Topics Covered in Part II of the EE5303 Module

- (a) Amplifiers
- (b) Oscillators
- (c) Mixers
- (d) Input/ output matching network (continued from Part 1)

### Key words:

- I. Stability, circle, stable/unstable region
- II. Gain, noise figures
- III. Multistage devices (Amplifier/mixers)
- IV. Reflection coefficients and impedances  
(Output/input/source/load)

## Sub-Topics:

- (a) Amplifiers
  - I. Stability check, stability regions
  - II. Unilateral design: maximum power/gain
  - III. Power gain, power gain circle
  - IV. Constant gain circle
  - V. Noise Figure
  - VI. Impedance matching (input/output matching network); Single-stub matching; working principle of filters

- (b) Oscillators
  - I. Un-Stability
  - II. Oscillating conditions
  - III. Max power

- (c) Mixers
  - I. Conversion loss
  - II. Up/down conversion, image frequency

